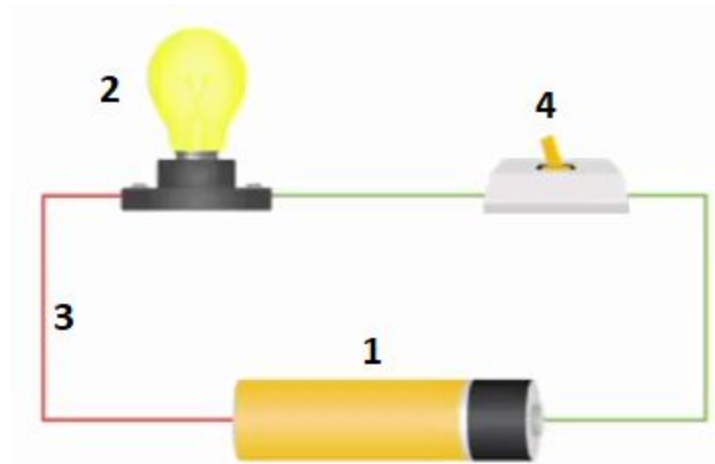


## Electric Circuits Notes

- Electric circuits have 4 features
  - 1. Source of electrical energy
    - Ex. battery
  - 2. Devices to use the electrical energy
    - Ex. light bulb
  - 3. Conducting wires
  - 4. Switch




- **Circuit diagrams** - drawings that represent an electric circuit
  - Common symbols used:

 Wire	 Bulb	 Open switch	 Resistor
 Closed switch	 Ammeter	 Battery	 Voltmeter

- When resistors resist the flow of electrical energy they turn it into 1 of 3 things
  - 1. Light
    - Ex. light bulb
  - 2. Mechanical energy
    - Ex. motor
  - 3. Thermal energy
    - Ex. space heater
    - All resistors do this in some form even if it's not their main purpose
      - Ex. A light bulb gets hot

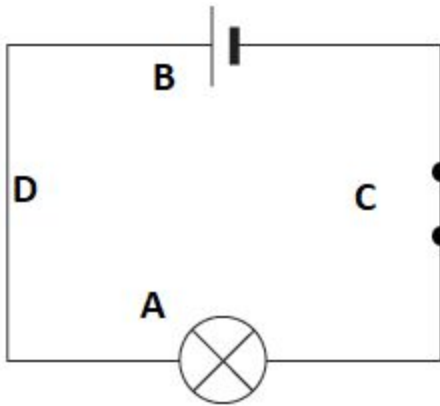- **Question:** Identify the parts of the circuit diagram labeled A, B, C, and D.




- A. bulb
  - B. battery
  - C. closed switch
  - D. wire
- Electric circuits fall under 3 main categories

Type	Definition	Example
Open circuit	A noncontinuous loop that prevents the flow of current	
Closed circuit	A continuous loop that allows the flow of current	
Short circuit	A disrupted circuit in which the current bypasses its proper path	

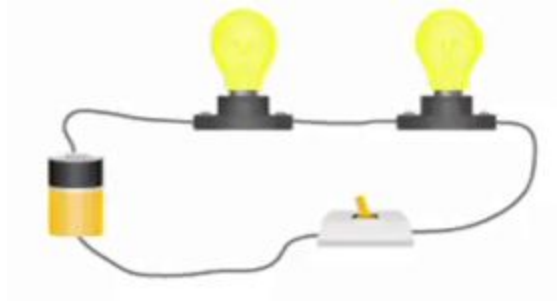- **Question:** Arrange the type of circuit in order of current flow from least to greatest.
    - Open, closed, short
- **Series circuit** - there is only one path for the current to flow

- Everything is connected in a single path



- Think of old Christmas lights. When one blows, the whole circuit is broken.
- As you add more and more bulbs to the circuit, each one gets dimmer.
  - Each bulb adds resistance, so it decreases the current
- They are simple to make though!

$$R_{eq} = R_1 + R_2 + R_3 + \dots R_n$$

- Formula:

- $R_{eq}$  = equivalent resistance (total resistance)

- Unit:  $\Omega$

- $R_n$  = resistance of nth resistor

- Unit:  $\Omega$

$$I = \frac{V}{R_{eq}} = \frac{V}{R_1 + R_2 + R_3 + \dots R_n}$$

- Formula:

- I = current

- Unit: A


- V = voltage

- Unit: V

- $R_{eq}$  = equivalent resistance (total resistance)


- Unit:  $\Omega$

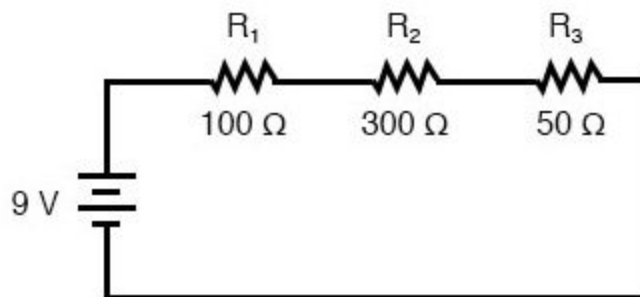- Question: Calculate the current for the circuit diagram below.



- Given:  $V = 9\text{ V}$ 
  - $R_1 = 100\ \Omega$
  - $R_2 = 300\ \Omega$
  - $R_3 = 50\ \Omega$
- Unknown:  $I = ?$
- Equations:  $I = \frac{V}{R_{eq}}$  and  $R_{eq} = R_1 + R_2 + R_3$
- Substitute:  $I = \frac{9\text{ V}}{R_{eq}}$  and  $R_{eq} = 100\ \Omega + 300\ \Omega + 50\ \Omega$
- Solve:  $I = \frac{9\text{ V}}{450\ \Omega} = 0.02\text{ A}$  and  $R_{eq} = 450\ \Omega$

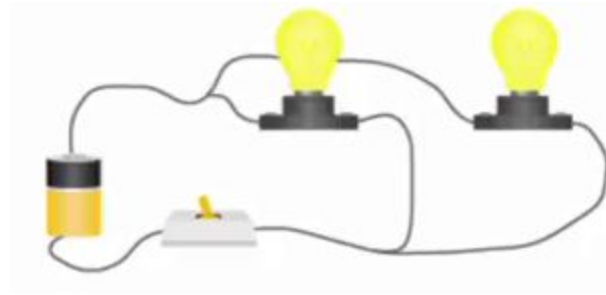- **Parallel circuits** - there are multiple branches for the current to travel



- If one branch is broken, the current can flow through the other branches instead
- These are like the new Christmas lights. If one bulb goes out, the other sections of the tree stay lit.
- All the bulbs shine at maximum brightness no matter what happens in the other branches.
- They are more difficult to build.


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$

- **Formula:**
  - $R_{eq}$  = equivalent resistance (total resistance)
    - Unit:  $\Omega$
  - $R_n$  = resistance of nth resistor
    - Unit:  $\Omega$

$$I = I_1 + I_2 + I_3 + \dots + I_n$$

- **Formula:**
  - $I$  = total current
    - Unit:  $\text{A}$
  - $I_n$  = current in nth branch
    - Unit:  $\text{A}$

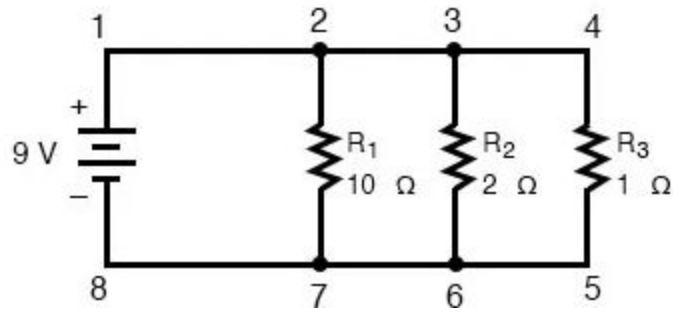- **Question:** Calculate the current for the circuit diagram below.



- Given:  $V = 9\text{ V}$   
 $R_1 = 10\ \Omega$   
 $R_2 = 2\ \Omega$   
 $R_3 = 1\ \Omega$
- Unknown:  $I = ?$
- Equations:  $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$  and  $I = \frac{V}{R_{eq}}$
- Substitute:  $\frac{1}{R_{eq}} = \frac{1}{10\ \Omega} + \frac{1}{2\ \Omega} + \frac{1}{1\ \Omega}$  and  $I = \frac{9\text{ V}}{R_{eq}}$
- Solve:  $\frac{1}{R_{eq}} = 0.1\ \Omega + 0.5\ \Omega + 1\ \Omega$  and  $I = \frac{9\text{ V}}{R_{eq}}$   
 $\frac{1}{R_{eq}} = 1.6\ \Omega$  and  $I = \frac{9\text{ V}}{R_{eq}}$   
 $R_{eq} = 0.625\ \Omega$  and  $I = \frac{9\text{ V}}{R_{eq}} = \frac{9\text{ V}}{0.625\ \Omega} = 14.4\text{ A}$