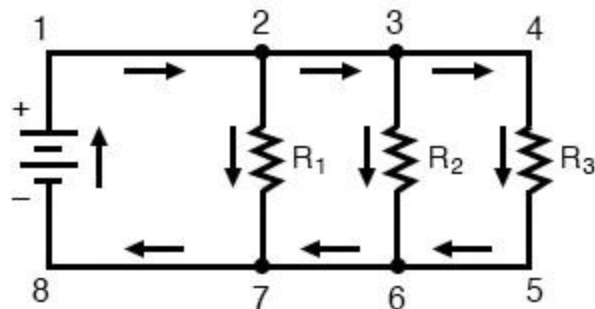


Lab: Circuit Design Notes

- Lab objective: "How do voltage, current, and resistance affect one another?"
- Using Ohm's Law:
 - Equation: $V = IR$
 - $V =$ voltage
 - Unit: V
 - $I =$ current
 - Unit: A
 - $R =$ resistance
 - Unit: Ω
 - Step 1: Rearrange Ohm's Law ($V = IR$) to what you are trying to solve for
 - $V = IR$
 - $I = \frac{V}{R}$
 - $R = \frac{V}{I}$
 - Step 2: Plug in your known variables
 - Step 3: Solve
 - Question: $V = 20\text{ V}$ and $R = 4\ \Omega$, find I .
 - Use: $I = \frac{V}{R}$
 - Plug in V and R : $I = \frac{20\text{ V}}{4\ \Omega}$
 - Solve: $I = 5\text{ A}$
- Calculating Resistance in a Circuit:
 - Step 1: Decide if the circuit is a series circuit or a parallel circuit
 - Remember: Series circuits only have one path
 - Remember: Parallel circuits have multiple paths
 - Step 2: Choose the right formula
 - For Series: $R_{eq} = R_1 + R_2 + \dots + R_n$
 - For Parallel: $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$
 - Step 3: Plug in your known resistances
 - Step 4: Solve
 - Question: The circuit below has three resistors: R_1 , R_2 , and R_3 . $R_1 = 5\ \Omega$, $R_2 = 3\ \Omega$, and $R_3 = 10\ \Omega$. Find the equivalent resistance of the circuit.



- Step 1: It is a parallel circuit because there are multiple paths the current can go.
 - Step 2: Use the formula for parallel circuits.
 - $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$
 - Step 3: Plug in our known resistances.
 - $\frac{1}{R_{eq}} = \frac{1}{5\Omega} + \frac{1}{3\Omega} + \frac{1}{10\Omega}$
 - Step 4: Solve
 - $\frac{1}{R_{eq}} = \frac{1}{5\Omega} + \frac{1}{3\Omega} + \frac{1}{10\Omega} = \frac{6}{30\Omega} + \frac{10}{30\Omega} + \frac{3}{30\Omega}$
 - $\frac{1}{R_{eq}} = \frac{19}{30\Omega}$
 - $R_{eq} = \frac{30\Omega}{19} = 1.6\Omega$
 - **Question:** If there is a 10 V battery in the circuit from the last example, what would the approximate current be?
 - Given: $V = 10\text{ V}$
 $R_{eq} = 1.6\Omega$
 - Unknown: $I = ?$
 - Equation: $I = \frac{V}{R}$
 - Substitute: $I = \frac{10\text{ V}}{1.6\Omega}$
 - Solve: $I = 6.25\text{ A}$
- Calculating Power in a Circuit
 - **Equation:** $P = IV$
 - $P = \text{power}$
● Unit: W
 - $I = \text{current}$
● Unit: A
 - $V = \text{voltage}$
● Unit: V
 - **Question:** A circuit has 5 A of current and 20 V of voltage running through it. How much power can a lightbulb that is attached to the circuit put out?
 - Given: $I = 5\text{ A}$
 $V = 20\text{ V}$
 - Unknown: $P = ?$
 - Equation: $P = IV$
 - Substitute: $P = (5\text{ A})(20\text{ V})$
 - Solve: $P = 100\text{ W}$
- Link:

<https://www.explorellearning.com/index.cfm?method=cExtAccessSecure.dspResource&ResourceID=398&certificate=authorizer%3dE2020%26userid%3dGizmos4Test%26expires%3d2020%2f03%2f24+13%3a47%3a57%26hash%3dmNKhINA5WvLBmQ49rcGAOA%253d%253d>