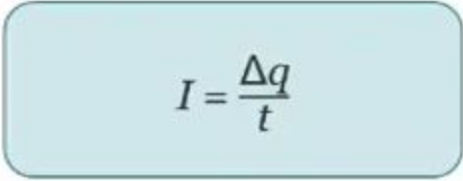


Ohm's Law Notes

- Electrons flow from places with higher electric potential energy to places with lower electric potential energy
 - Why? Electricity is like a falling object.
 - Things fall from higher gravitational potential energy to places with lower gravitational energy
 - i.e. Things fall from high to low
- **Current** - the continuous flow of electric charge
 - Also known as the rate at which a charge moves through a conductor


$$I = \frac{\Delta q}{t}$$

- **Equation:**
 - I = current
 - Unit: ampere (A)
 - Δq = change in electric charge
 - Unit: C
 - t = time
 - Unit: s
- **Question:** It takes 10.0 seconds for 15 coulombs of charge to flow through a wire. How much current is flowing through it?
 - Given: t = 10.0 s
 $\Delta q = 15 \text{ C}$
 - Unknown: I = ?
 - Equation: $I = \frac{\Delta q}{t}$
 - Substitute: $I = \frac{15 \text{ C}}{10.0 \text{ s}}$
 - Solve: I = 1.5 A
- **Electric circuit** - a path through which electric charges or current can travel
- **Voltage** - the difference in electric potential between two spots
 - Unit: Volt (V)
 - Current flows from higher electric potential to lower electric potential
 - The bigger the voltage the more current
- **Resistance** - the tendency of a material to oppose the flow of charges
 - Unit: ohm (Ω)
 - The bigger the resistance the less current
 - You can change a wire's resistance by changing the wire's
 - Thickness
 - Length
 - Temperature
 - Any device that uses electricity has resistance

- **Question:** A thick wire has _____ resistance than a thin wire.
 - Less
- **Question:** A long wire has _____ resistance than a short wire.
 - More
- **Question:** A cool wire has _____ resistance than a warm wire.
 - Less
- Ohm's Law - current is equal to voltage divided by resistance

$$I = \frac{\Delta V}{R}$$

- **Formula:**
 - I = current
 - Unit: A
 - ΔV = change in voltage
 - Unit: V
 - R = resistance
 - Unit: Ω
- **Question:** What is the current in a circuit with a 9.0 V battery and a 1.5 Ω resistor?
 - Given: $\Delta V = 9.0 \text{ V}$
 $R = 1.5 \Omega$
 - Unknown: $I = ?$
 - Equation: $I = \frac{\Delta V}{R}$
 - Substitute: $I = \frac{9.0 \text{ V}}{1.5 \Omega}$
 - Solve: $I = 6 \text{ A}$
- **Question:** How does the current in a circuit change if the resistance is tripled?
 - The current is $\frac{1}{3}$ what it used to be.
 - Plug in 3 for R and see what happens to I